



Transistor Sizing: How to Control the Speed and Energy Consumption of a Circuit

Jo Ebergen, Jonathan Gainsley,
Paul Cunningham

Async Design Group

Sun Labs

SML2004-0325

Public Information



Transistor Sizing: How to Control the Speed and Energy Consumption of a Circuit

Jo Ebergen, Jonathan Gainsley, Paul Cunningham
Asynchronous Design Group
Sun Labs

Introduction


- Transistor sizes (widths) determine
 - Speed of circuit
 - Energy consumption
 - Total area of circuit
 - Satisfaction of delay constraints
- Success or failure

How Do I Pick Transistor Widths?

- To optimize for speed?
- To optimize for energy?
- Automatically and quickly?
- Does a circuit have a speed limit?
- Is there a trade-off between speed and energy?
- How do I compare circuits built for different technologies?


An Example

 - Given desired gate delays s_0 , s_1 , and s_2 , fixed latch load L and fixed wire load W
 - How do I find the sizes x_0 , x_1 , and x_2 ?
- Cycle time = $s_0 + s_1 + s_2$. What is minimum?



The Delay Model

 - Defines relationship between gate sizes and delays
- Capacitance driven by gate in time s
= sum of all capacitances on node
 - s = gate delay
 - x = drive strength [capacitance/time]



$$s_0 \cdot x_0 = C_{dif0} + C_L + C_{in1}$$

- Input and diffusion capacitances are linear functions of drive strength [Idea of Logical Effort]

Units


- Unit of capacitance
 - κ = Input cap of min. sized inverter
 - All fixed loads must be converted
- Unit of delay s (for stepup or slope)
 - τ = Delay of ideal inverter, with no diffusion capacitance, driving copy of itself.
 - $FO4 = 5 * \tau$
- Unit of drive strength x (as in 4X, 8X)
 - κ / τ = Capacitance per time unit

Technology Independence

- Units κ and τ depend on technology
- Ex: TSMC 180nm, $\tau = 17\text{ps}$ (FO4 = 85ps)
- Equations are independent of technology
- Allows comparisons of circuits in different technologies
- Warning: wire loads do not scale linearly

Logical Efforts

 - Let me find gate capacitances as function of size x
- Input and diffusion capacitances are proportional to drive strength
- Logical Effort of input (LE_{in}) = input capacitance per unit of drive strength
- Logical Effort of output (LE_{out}) = diffusion capacitance per unit of drive strength











Properties of Logical Effort

- Logical Effort = “effort” to compute logic function
- Logical effort is a time constant [$\kappa / (\kappa / \tau) = \tau$]
- LE_{out} = time to load diffusion capacitance of gate
 - parasitic delay
- LE_{in} = time to load input capacitance of gate (with the same drive strength)
- Logical efforts can be found from transistor diagram or empirically


Examples

- Some gates and their logical efforts

        

Back To Example

 - Use delay model, now with Logical Efforts



$$\begin{array}{l}
 s_0 * \begin{bmatrix} x_0 \end{bmatrix} = \begin{bmatrix} 2 * x_0 + 1 * x_1 \end{bmatrix} \\
 s_1 * \begin{bmatrix} x_1 \end{bmatrix} = \begin{bmatrix} 1 * x_1 + 1 * x_2 \end{bmatrix} + \begin{bmatrix} L \end{bmatrix} \\
 s_2 * \begin{bmatrix} x_2 \end{bmatrix} = \begin{bmatrix} 4/3 * x_0 \end{bmatrix} + \begin{bmatrix} 1 * x_2 \end{bmatrix} + \begin{bmatrix} W \end{bmatrix}
 \end{array}$$

In Matrix form: $S * \underline{x} = T * \underline{x} + \underline{C}$

In General

- $S \cdot x = T \cdot x + C$
- S = diagonal matrix of gate delays
- x = vector of drive strengths
- T = logical effort matrix
 - $T_{ij}=0$ no connection from gate i to gate j
 - $T_{ij} \neq 0$ connection from gate i to gate j
 - Describes topology of circuit
- C = vector of fixed loads
- Equations can be extracted from netlist


Now What?

- Does a solution x exist for given S , T , and C ?
- How do I compute solution for x efficiently?
- How to choose delays S ?
- Special case: equal gate delays
 - Simpler model: $s*x = T*x + C$
 - Path delay = ($\#$ gates)* s
 - Easy for satisfying delay constraints
 - More accurate

How To Compute Drive Strengths?

- Many ways to solve $s^*x=T^*x+C$
- Easiest is iteration
- Let $f(x)=(T^*x+C)/s$
- $x(0)=0$
- Repeat $x(i+1)=f(x(i))$ until convergence
- Converges quickly, if you choose s well

An Example

 


$$x_2 = (x_2 + 10 + 4/3 * x_0) / 3$$

$$x_1 = (x_1 + 10 + x_2) / 3$$

$$x_0 = (2 * x_0 + x_1) / 3$$

x2:	0	3.66	4.69	4.74	..
x1:	0	4.89	5.23	5.25	..
x0:	0	2.3	2.41	2.41	..


 


Critical Delay

- Only for circuits with cycles
 - Almost all async control ckts have cycles!
- Equal gate delay: $s^*x = T^*x + C$
- **Critical delay (cs) of circuit
= largest real eigenvalue of T**
- Feasible solution exists iff s is larger than critical delay ($s > cs$)
- Critical delay is independent of fixed loads C
- Sizing algorithm converges if $s > cs$


Total size and critical delay

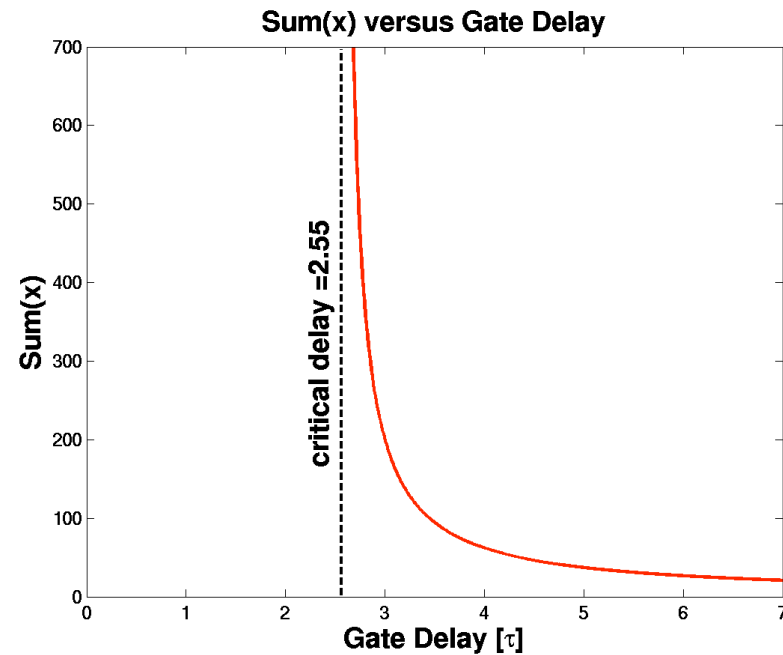 - Total size ($\sum x$'s) as function of gate delay
- Size grows as $C/(s-cs)$



Critical Delay and Limits

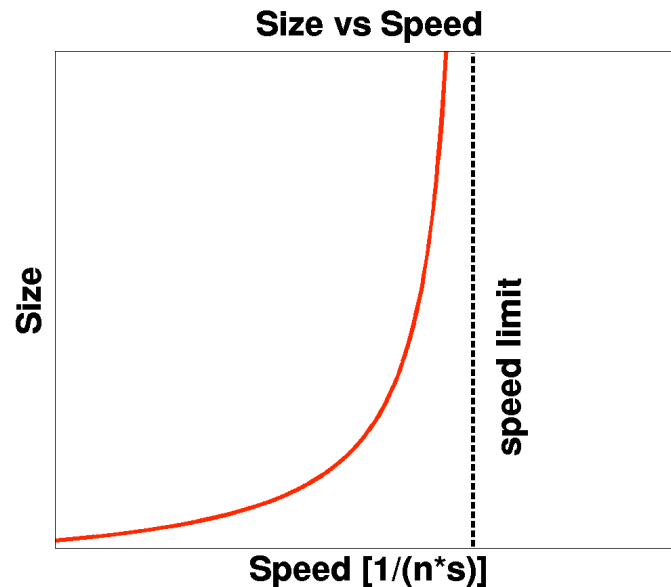- Critical delay defines lower bound for gate delay, assuming equal gate delays
- Critical delay (cs) and # gate delays (n) in cycle define speed limit for throughput $=1/(n*cs)$



Energy Estimation

- Dynamic Energy
 - Due to (dis)charging capacitance C
 - Proportional to $C \cdot V^2$
- Short-Circuit Energy
 - Due to crossover current
 - If input and output slope are equal, short-circuit energy $\approx \alpha \cdot$ dynamic energy consumption [Veendrick84]
- Static Energy
 - Due to leakage currents
 - Ignore for now

Units



- Unit of energy
 - ϵ = energy spent by ideal minimum inverter, excl. diffusion capacitance, driving a minimum inverter
- “Energy spent” = energy lost in resistors
- Unit ϵ depends on technology, but equations do not
- Can be determined empirically
 - $\epsilon=2.9\text{fJ}$ in TSMC 180nm, 1.8V.

More On Energy Estimation

- In equal-gate-delay model
- $s^*x = T^*x + C$
- Energy spent by gate \propto total output cap
- Energy spent by gate $i \propto (T^*x + C)_i = s^*x_i$
- Let p_i be activity index of gate i in an execution
- Total energy spent in an execution = $\sum_i p_i^*s^*x_i$


An Example: Magic Clock

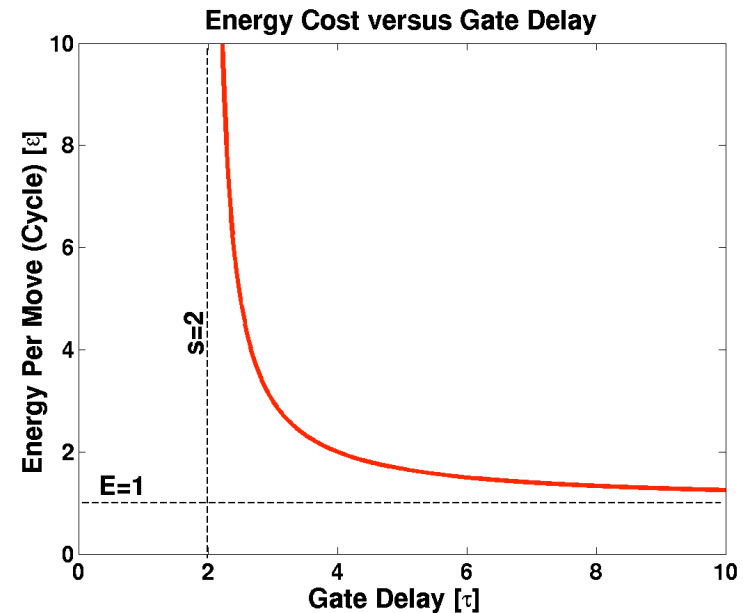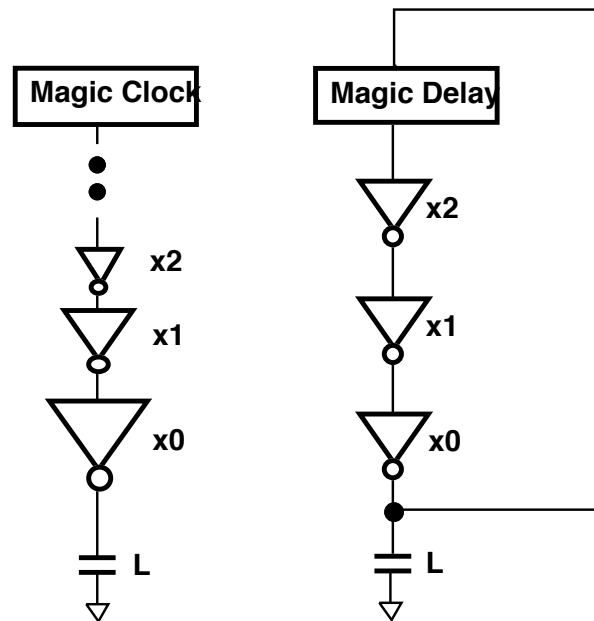- Every inverter has the same delay
- Control must charge and discharge load L
- $E = 1 + 2/(s-2)$ per unit load
- For equal delays, the best you can do




Comparing Circuits

 - Independent of process technology
- Example: asynchronous controls of ripple FIFO
- How do different implementations compare in terms of energy versus performance?




The Implementations


- Chain of Rendezvous (COR):

 

- asP*:

 

- GasP:

 


More Implementations

- Berkel's single-track handshake
- Singh & Nowick's High-Capacity Pipeline
- IPCMOS by Schuster et al
-
- Magic clock
 - the lower bound and the ideal “synchronous” implementation.


Critical Times

Ckt	Critical Gate Delay	# Gates in Cycle	Critical Cycle Time
Magic Clock	2.0	6 ¹⁾	12
GasP	2.42	6	14.52
IBM IPCMOS ²⁾	2.51	14	35.14
Singh-Nowick	3.38	8	27.04
asP*	3.95	8	31.6
Berkel's single-track	4.21	6	25.26
Chain of C-elements	4.56	3 ³⁾	13.68

A Price/Performance Comparison

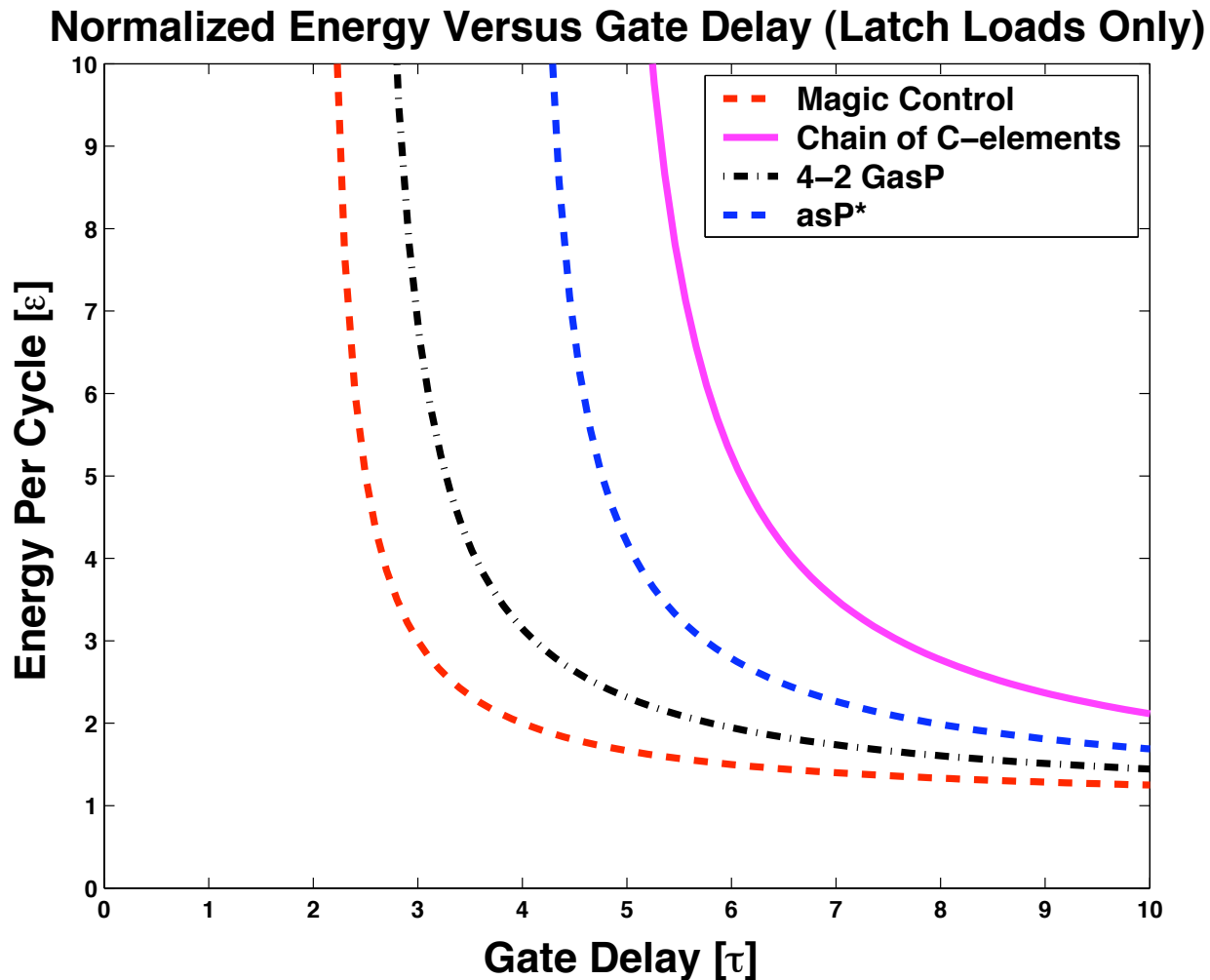

A Price/Performance Comparison

 

It's (Like) The Economy, Stupid

- Moving charges in circuit
= Moving capital goods in economy
- Open input-output model
 - “Gate” = economic sector
 - “Capacitance” = demand for capital goods
 - “Drive strength” = supply of capital goods per time unit
 - “Energy” = total cost of capital goods
- Wassily Leontief (1906-1999)
- Has many applications
- Abundant literature
- A chip is like an economy

Summary

- Simple model for calculating transistor sizes
- Simple and efficient algorithms
- Good results obtained so far with equal gate delays
- **Critical delay** gives a price/performance characteristic for a control circuit
- Gives insight into speed-energy trade-offs
- Allows comparisons of circuits independent of process technology