





# Squaring the FIFO in GasP

**Jo Ebergen**  
**Asynchronous Design Group**  
**Sun Labs**



# Introduction

- A novel method for asynchronous design
  - GasP circuits
  - Notation for sequencing events
  - Logical Effort for uniform delays
- Example: Square FIFO
- Throughput of 1.56 GDI/s in 0.35u






## Related Work

- **asP\* FIFO** of Molnar et al.
- **Self-resetting domino**
- **IBM's Interlocked Pipelined CMOS**
- **Erik Brunvand's Square FIFO**




 
# A GasP Module

- Control circuit = network of GasP modules
- GasP module realizes
  - Sequencing
  - Synchronization




# Inside a GasP Module

  


# A Sequence of Events

a → b

 


# Delay Assignment of 4

a → b


 


↓

 

# Delay Assignment of 2


a ← b

  



# A Simple Translation

- State: wire + keeper
- Event: GasP module

$$P = (a \rightarrow Q)$$

 


$$P = (a \rightarrow Q) \\ | b \rightarrow R)$$

  

 
# A One-Stage FIFO

```
Stage1 =  
state E where  
  E = (a -> F)  
  F = (b -> E)  
end
```



 
# A Two-Stage FIFO (1)

```
Stage1 =  
state E where  
    E = (a -> F)  
    F = (b -> E)  
end
```



 
```
Stage2 =  
state E where  
    E = (b -> F)  
    F = (c -> E)  
end
```





# A Two-Stage FIFO (2)


Stage1 & Stage2

 

# A Peephole Optimization

  


# A Square FIFO

 

- Latency =  $2 * \sqrt{N}$  for capacity=N
- Low Power
- Max throughput for large range of occupancies
- Simple layout



# Data Path of Square FIFO

 


# Implementation

- Each cell is a Finite State Machine
- Columns are linear FIFOs
- Top row and bottom row are special




# Implementation of Cell 1

 


```

Cell1 =
state E0 where
  E0 = (r0 -> F0)
  F0 = (r1 -> E0
        | rr1 -> E1)
  E1 = (rr0 -> F1)
  F1 = (d1 -> E0)
end

```

 

# Complete Implementation for Control

 


# Experimental Results


- Fabricated in 0.35 $\mu$  CMOS through MOSIS
- Ring with two 5X5 and two 2X5 FIFOs
- Transistor sizing
- No bottlenecks
- First chip failed
  - Wire lengths grossly underestimated
- Second chip works fine



# Throughput

 

# Power Consumption

 

# Concluding Remarks

- Speed, Speed, Speed
- Simple, Simple, Simple
- GasP, a minimal control primitive
- Control circuit = composition of FSMs
  - Event : GasP module
  - State : wire + keeper
- Careful sizing
  - Logical Effort
  - Wire estimates
- More testing needed



