

Circuits Without Clocks: What Makes Them Tick?

**Jo Ebergen
Sun Microsystems Laboratories
jo.ebergen@sun.com**



A Historical Perspective

- **Clocked versus clockless**
- **The first computers: clocked or clockless?**
- **ENIAC('46), ACE('46), EDVAC ('46)**
- **Enablers: Switching Theory and FSMs**
- **A BIG problem: making reliable computers**
- **Clock is convenient in design and verification**
- **Terminology: non-synchronous, asynchronous, speed-independent, self-timed, delay-insensitive**

Why No Clock?

- **Speed**
 - **Average vs worst-case behavior**
- **Avoid timing problems related to clock**
 - **Synchronization problem**
 - **Clock distribution, skew, jitter**
- **Modularity**
 - **Reusability**
 - **Composability**
 - **Incremental improvement**

An Example: Macromodules ('66-'74)

  


More: Why No Clock?

- **Low power**
 - **Portable electronics**
 - **Budget constraint: total energy, not cycle time**
- **Architectural freedom**
 - **Concurrency at any grain size**
- **Robustness**
 - **Correct operation over a large range of process, voltage, and temperature variations**
- **Reduced electromagnetic radiation**
 - **Spread spectrum versus isolated peaks**


A Live Demo

 - Pipelined “food” processing
- Clocked and clockless version




Clocked “Food Processing”

 - **TICK:** process food
- **TOCK:** move plate to successor




Clockless “Food Processing”

 - Two types of plates
- Red plate = stage with data item
- White plate = empty stage
- Red plates move forward
- White plates move backward



Repeat These Actions

 - **TAKE:** Take RED plate from predecessor
(and give WHITE plate)
- **EAT:** Process food
- **GIVE:** Give RED plate to successor
(and take WHITE plate)



To Notice


- **Clock period must be long enough for slowest person for worst food**
- ***Clockless pipeline adjusts speed to person and food being processed***
- **Clocked pipeline spends energy with every tick or tock, even when there is no food on plate**
- ***Clockless pipeline spends energy only when food must be processed***

More To Notice

- **Clocked pipeline must have the same frequency as the source and sink, to prevent overflow or underflow**
- ***Clockless pipeline has automatic overflow and underflow protection***

FIFOs

 - **FIFOs as a basis for pipelines**
- **Simple local communication**




- **Red plates move to the right**
- **White plates move to the left**

Local Communication

- Synchronization at each boundary
- Only one rule:

 
**IF (left plate is red AND right plate is white)
THEN exchange plates**



**instantaneous
event**

An Implementation Scheme

- Using bundled data signaling

 

Control Path

Drivers

Data Path =
latches or flip-flops
+ logic

About Bundled Data Signaling




- **Similar to clocked design, but with local “clocks”**
- **Control modules produce “clock” signal**
 - **when needed**
 - **where needed**
- **“Clock” signal can be**
 - **level signal**
 - **transition signal**
 - **pulse signal**
- **Type of latch or flip-flop depends on “clock” signal**

Many Implementations

- **Many circuits can implement local synchronization**
 - **Muller C-elements**
 - **asP* circuits**
 - **GasP modules**
 - **Many others...**
- **Challenge is to find circuits that**
 - **have small delay**
 - **have small area**
 - **consume little energy**
 - **can do pipelines with Branch, Merge, Fork, Join, etc**


Muller C-Element

   - Also known as Rendezvous or JOIN
- David Muller (60s)
- If both inputs are 1 (0), then output becomes 1 (0)
 - If inputs differ, output remains the same
- C-element = “AND” of transitions




About Speed

- **Forward latency of stage**

 

- **Reverse latency of a stage**

 


- **Cycle time of a stage: $L_f + L_r$**
- **Forward latency of linear FIFO: $n * L_f$**
- **Reverse latency of linear FIFO: $n * L_r$**
- **Throughput of FIFO: $1 / (L_f + L_r)$**

Measuring Speed

- **Throughput of ring FIFOs**


- **“Token-limited”**

Red plates never have to wait

 

- **“Bubble-limited”**


White plates never have to wait

 

- **Limited by an interface stage**


Speed Example

 - Measurement from chip, asP* FIFO (600nm, 3.3V)




Power Example

 - Measured from chip, asP* FIFO (600nm, 3.3V)
- Power proportional to throughput!



A Energy/Performance Comparison

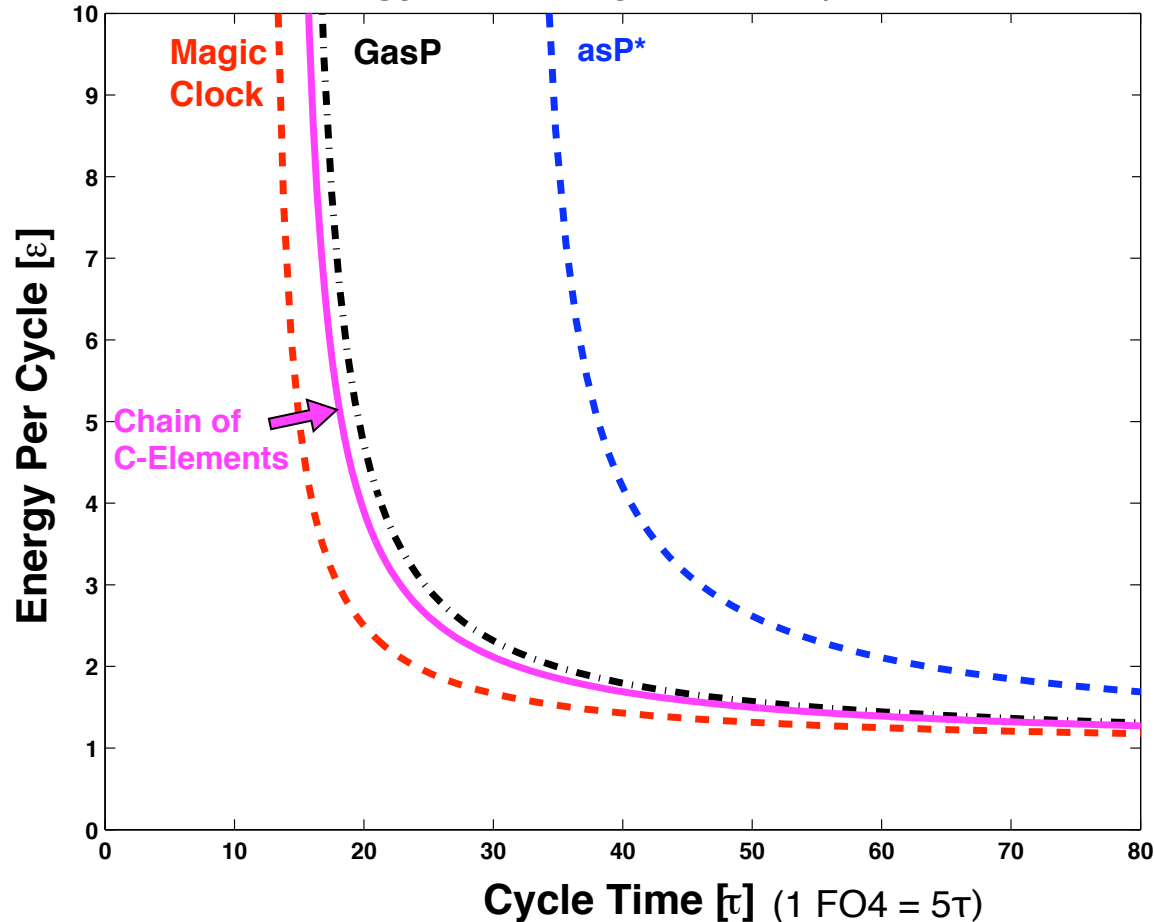
Normalized Energy Versus Cycle Time (Latch Loads Only)



 1. Assumption: All gates have equal delay
2. Magic clock is infinite string of inverters with min cycle time of 6 gate delays
3. C-element FIFO has cycle time of 3 gate delays
4. In TSMC 180nm, $\tau = 14\text{ps}$, $\epsilon = 2.6\text{fJ}$.



Robustness

- Max throughput vs supply voltage and temperature
- C-element FIFO (600nm, 3.3V)




Reduced Radiation

  - Frequency spectrum of the same chip operating in sync and async mode



Average-Case Speed

- From asP* counterflow pipeline chip

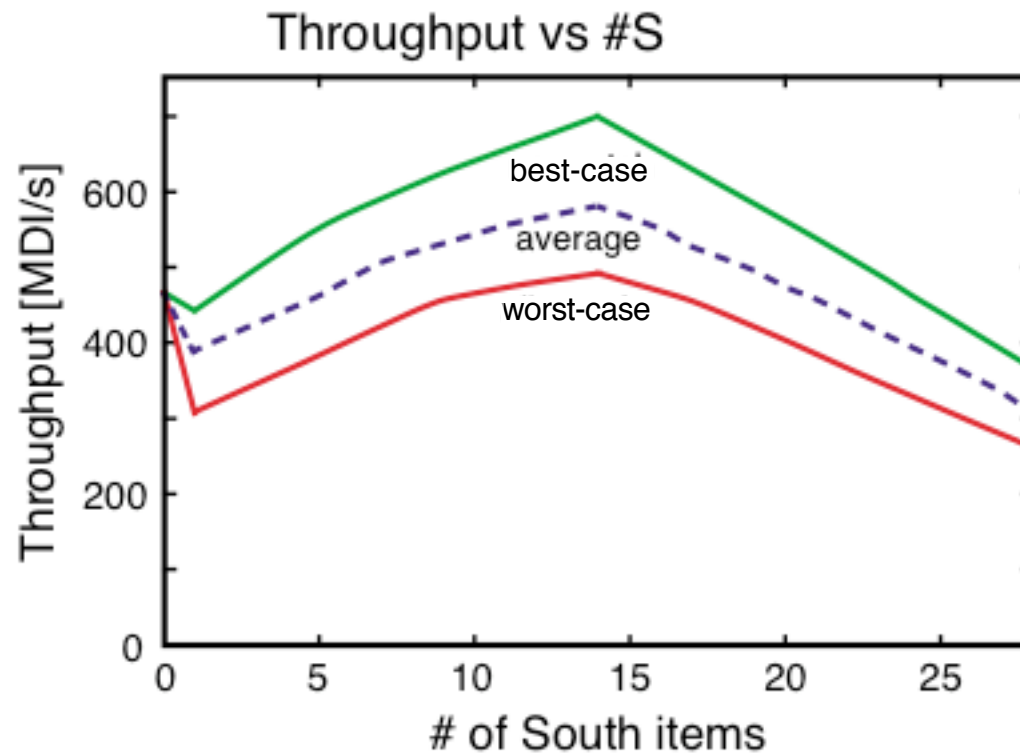

Architectural Freedom

- **Can more freedom lead to better FIFOs?**
- **Better = lower power?**
- **Better = less latency?**
- **More concurrency?**
- **Different grain sizes (i.e. cycle times)?**

Concluding Remarks

- **Sun's UltraSPARCIII has async FIFOs**
- **Elsewhere..**
 - **Philips, IBM, Intel, ..**
 - **Academia**
 - **Start-ups**
- **Many challenges remain**
 - **CAD tools**
 - **Education**
 - **Creating order in "chaos of concurrency"**

Resources

- **Async Design Group at Sun Labs**
 - research.sun.com/async/
- **Async Logic Home Page**
 - www.cs.man.ac.edu/async/
- **Ivan Sutherland's Turing Award lecture 1989**
- **“Computers Without Clocks” Scientific American, Aug. 2002**
- **ASYNC conference series**